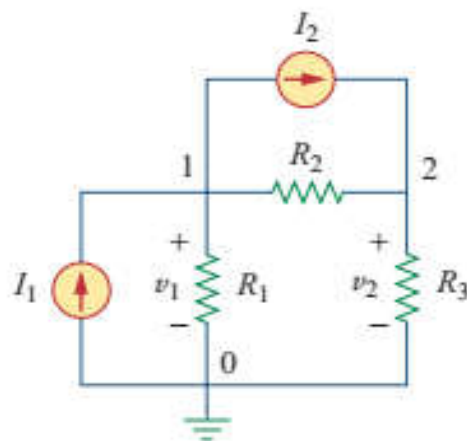



## Nodal Analysis

- 1-Determine the number of nodes within the network.
- 2-Label each remaining node with a subscripted value of voltage:  $V_1$ ,  $V_2$ , or  $V_a$ ,  $V_b$ , and so on.
- 3-Define one of the nodes as a reference node (that is, a point of zero potential or ground).
- 4-Apply Kirchhoff's current law at each node except the reference node.
- 5-Solve the resulting equations for the nodal voltages

Now, consider for example the circuit of figure shown below



Steps: (1-3)

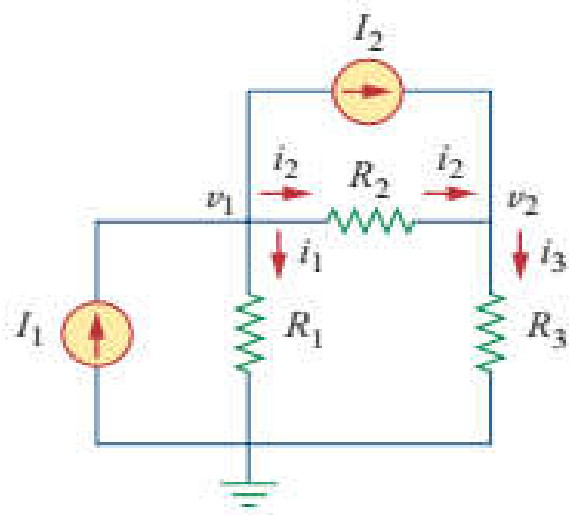

$$V_3=0$$

At node (1), Applying KCL:

$$I_1 - i_1 - i_2 - I_2 = 0 \quad \dots (1)$$

$$i_1 = \frac{v_1 - v_3}{R_1}, \quad i_2 = \frac{v_1 - v_2}{R_2},$$

$$v_3=0;$$

$$i_1 = \frac{v_1}{R_1}$$

$$I_1 - \left(\frac{v_1}{R_1}\right) - \left(\frac{v_1 - v_2}{R_2}\right) - I_2 = 0 \quad \dots (2)$$

At node (2),

$$I_2 + i_2 - i_3 = 0$$

$$I_2 + \left( \frac{v_1 - v_2}{R_2} \right) - \left( \frac{v_2 - v_3}{R_3} \right) = 0 \quad \dots (3)$$

Simplifying the two equations (2 and 3) then:

$$I_1 - I_2 = v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{1}{R_2} v_2 \quad \dots (4)$$


$$I_2 = v_2 \left( \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{1}{R_2} \quad \dots (5)$$

Note: the variables are  $v_1, v_2$ .

(Format Approach) هذه الصيغة تسمى

So, solving equations 4 and 5 simultaneously to find the values of  $v_1, v_2$ .

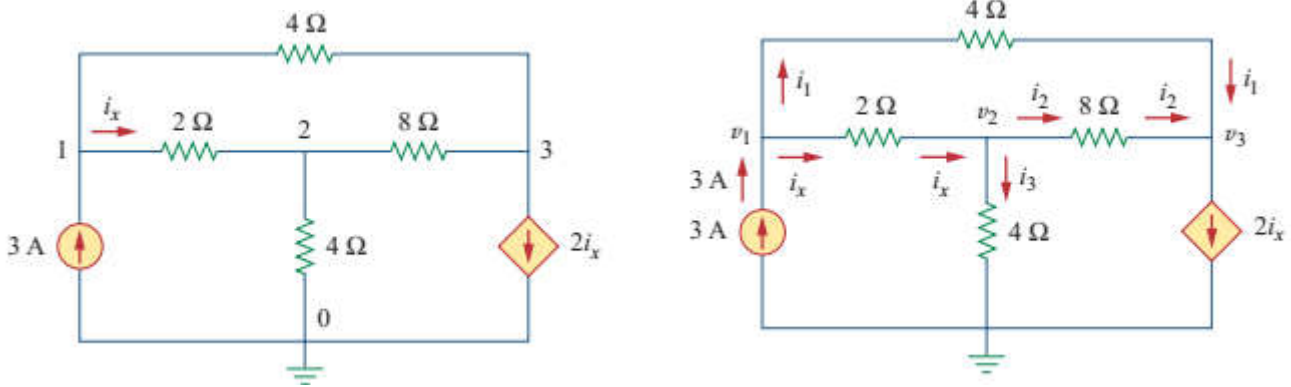Example: Calculate the node voltages of figure shown below:



$$\text{Solution: } [12 = 3v_1 - 3v_3 + 6v_1 - 6v_2] * \frac{1}{3}$$

At node 1,

$$3 = i_1 + i_x \quad \Rightarrow \quad 3 = \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2}$$

Multiplying by 4 and rearranging terms, we get

$$3v_1 - 2v_2 - v_3 = 12 \quad (1)$$

At node 2,

$$i_x = i_2 + i_3 \quad \Rightarrow \quad \frac{v_1 - v_2}{2} = \frac{v_2 - v_3}{8} + \frac{v_2 - 0}{4}$$

Multiplying by 8 and rearranging terms, we get

$$-4v_1 + 7v_2 - v_3 = 0 \quad (2)$$

At node 3,

$$i_1 + i_2 = 2i_x \quad \Rightarrow \quad \frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = \frac{2(v_1 - v_2)}{2}$$


Multiplying by 8, rearranging terms, and dividing by 3, we get

$$2v_1 - 3v_2 + v_3 = 0 \quad (3)$$

Solving the three equations, then

$$v_1 = 4.8 \text{ V}, \quad v_2 = 2.4 \text{ V}, \quad v_3 = -2.4 \text{ V}$$

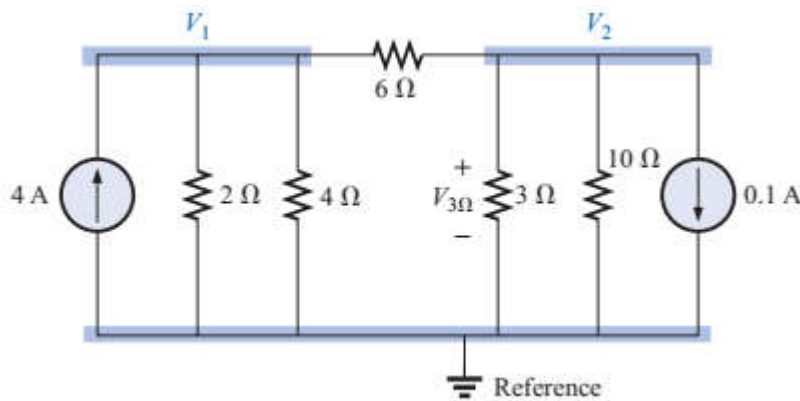Example:- Find the voltage across the 3-Ω resistor of figure below, Using nodal analysis.



Solution:

$$\left(\frac{1}{2\Omega} + \frac{1}{4\Omega} + \frac{1}{6\Omega}\right)V_1 - \left(\frac{1}{6\Omega}\right)V_2 = +4\text{ A}$$

$$\left(\frac{1}{10\Omega} + \frac{1}{3\Omega} + \frac{1}{6\Omega}\right)V_2 - \left(\frac{1}{6\Omega}\right)V_1 = -0.1\text{ A}$$

$$\frac{11}{12}V_1 - \frac{1}{6}V_2 = 4$$

$$-\frac{1}{6}V_1 + \frac{3}{5}V_2 = -0.1$$


$$11V_1 - 2V_2 = +48$$

$$-5V_1 + 18V_2 = -3$$

Solving these equations:

$$V_2 = 1.101\text{ volt.}$$

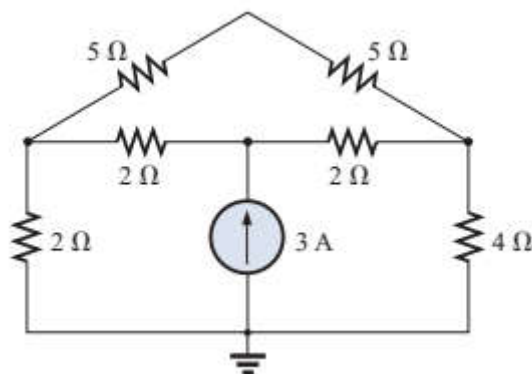
HW/using Nodal analysis , determine the potential across the  $4\Omega$  resistor in figure below.



2-

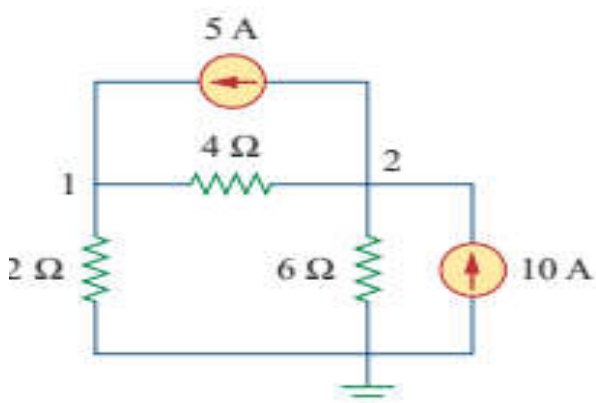**Example 3.1**


Calculate the node voltages in the circuit shown in Fig. 3.3(a).



Find the voltages at the three nonreference nodes in the circuit of Fig. 3.6.


3-

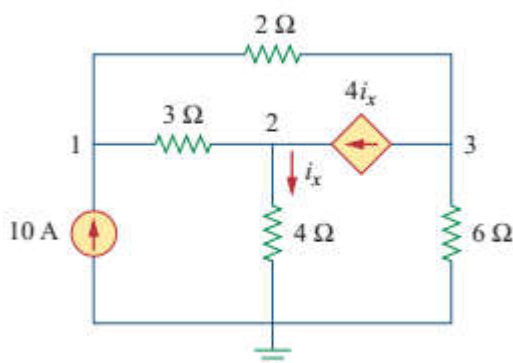**Answer:**  $v_1 = 80\text{ V}$ ,  $v_2 = -64\text{ V}$ ,  $v_3 = 156\text{ V}$ .



## Nodal Analysis with Voltage Sources

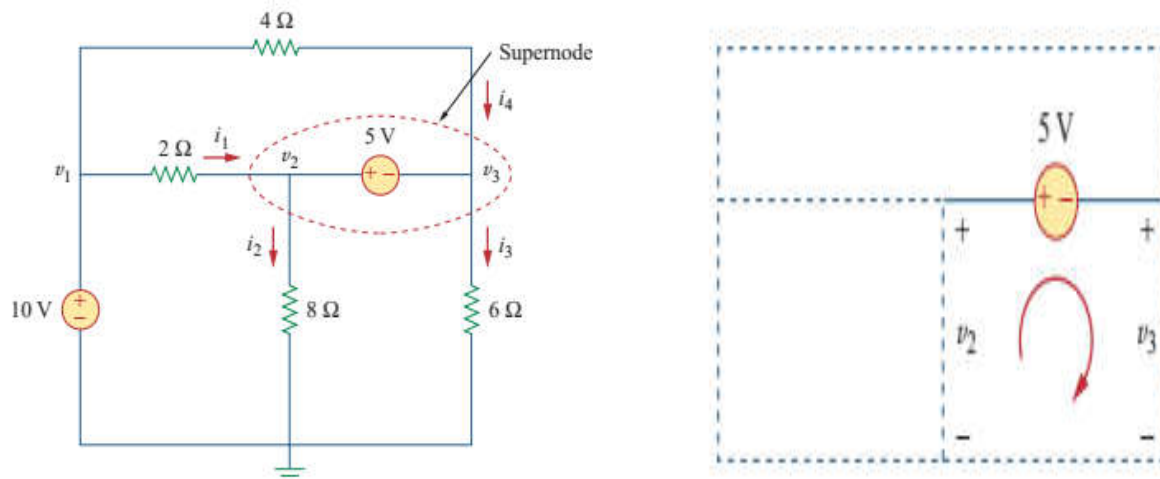Example: for the circuit shown below, find the values of  $v_1$ ,  $v_2$ , and  $v_3$ .



■ **CASE 1** If a voltage source is connected between the reference node and a nonreference node, we simply set the voltage at the nonreference node equal to the voltage of the voltage source. In Fig. 3.7, for example,

$$v_1 = 10 \text{ V} \quad (3.10)$$

■ **CASE 2** If the voltage source (dependent or independent) is connected between two nonreference nodes, the two nonreference nodes

form a *generalized node* or *supernode*;


A **supernode** is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.

$$i_1 + i_4 = i_2 + i_3$$

$$\frac{v_1 - v_2}{2} + \frac{v_1 - v_3}{4} = \frac{v_2 - 0}{8} + \frac{v_3 - 0}{6}$$

$$-v_2 + 5 + v_3 = 0 \quad \Rightarrow \quad v_2 - v_3 = 5$$

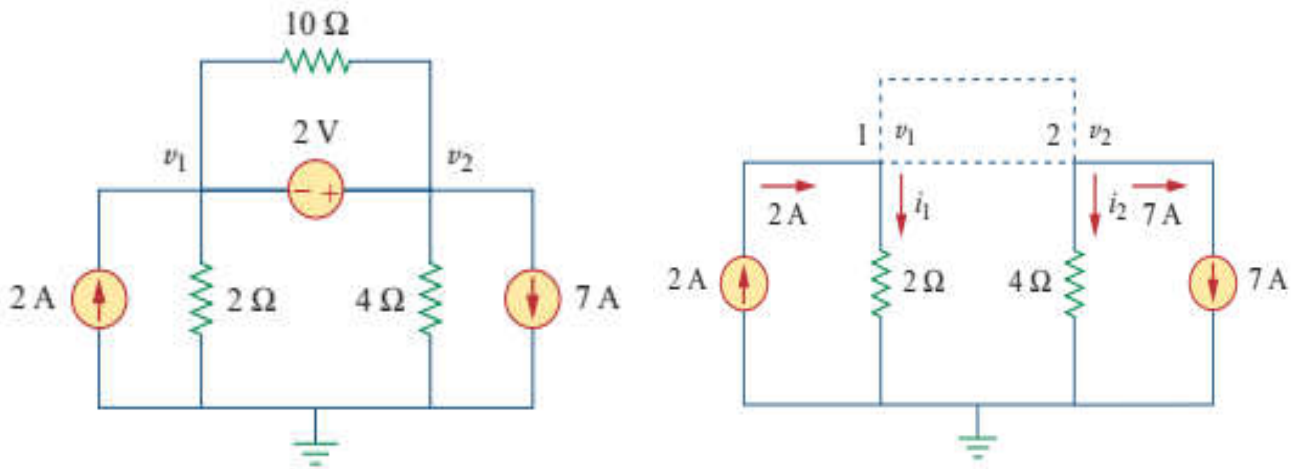Example:- for the circuit shown below, determine the node voltages.



Solutions:-

The supernode contains the 2-V source, nodes 1 and 2, and the 10-Ω resistor. Applying KCL to the supernode as shown in Fig. 3.10(a) gives


$$2 = i_1 + i_2 + 7$$

Expressing  $i_1$  and  $i_2$  in terms of the node voltages

$$2 = \frac{v_1 - 0}{2} + \frac{v_2 - 0}{4} + 7 \quad \Rightarrow \quad 8 = 2v_1 + v_2 + 28$$

$$v_2 = -20 - 2v_1$$

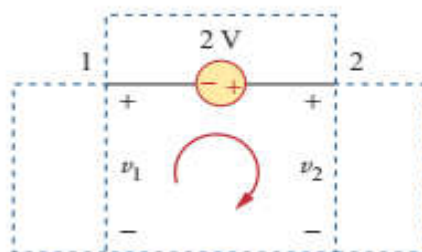To get the relation between  $v_1$  and  $v_2$ , apply KVL to the circuit in figure below.



$$-v_1 - 2 + v_2 = 0 \quad \Rightarrow \quad v_2 = v_1 + 2$$




$$v_2 = v_1 + 2 = -20 - 2v_1$$

or

$$3v_1 = -22 \quad \Rightarrow \quad v_1 = -7.333 \text{ V}$$


and  $v_2 = v_1 + 2 = -5.333 \text{ V}$ . Note that the  $10\text{-}\Omega$  resistor does not make any difference because it is connected across the supernode.

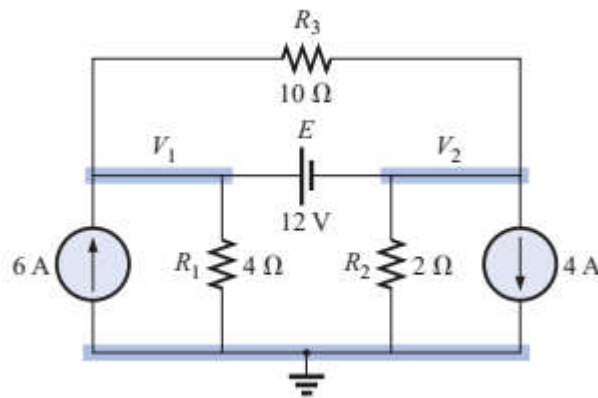HW//For the circuit shown below, determine the node voltages.


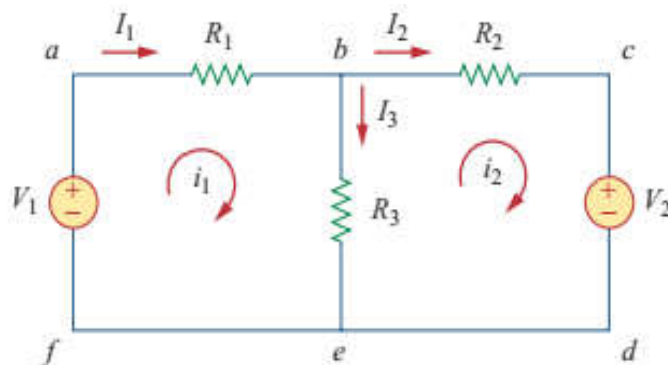
# Mesh Analysis

A **mesh** is a loop which does not contain any other loops within it.



- In the figure shown below, for example, paths(abefa) and (bcdeb) are meshes, but path (abcdefa) is not a mesh.
- The current through a mesh is known as mesh current.
- Applying KVL to find the mesh currents in a given circuit.

## Steps to Determine Mesh Currents:

1. Assign mesh currents  $i_1, i_2, \dots, i_n$  to the  $n$  meshes.
2. Apply KVL to each of the  $n$  meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting  $n$  simultaneous equations to get the mesh currents.

$$-V_1 + R_1 i_1 + R_3(i_1 - i_2) = 0$$

or

$$(R_1 + R_3)i_1 - R_3 i_2 = V_1$$


For mesh 2, applying KVL gives

$$R_2 i_2 + V_2 + R_3(i_2 - i_1) = 0$$

or

$$-R_3 i_1 + (R_2 + R_3)i_2 = -V_2$$

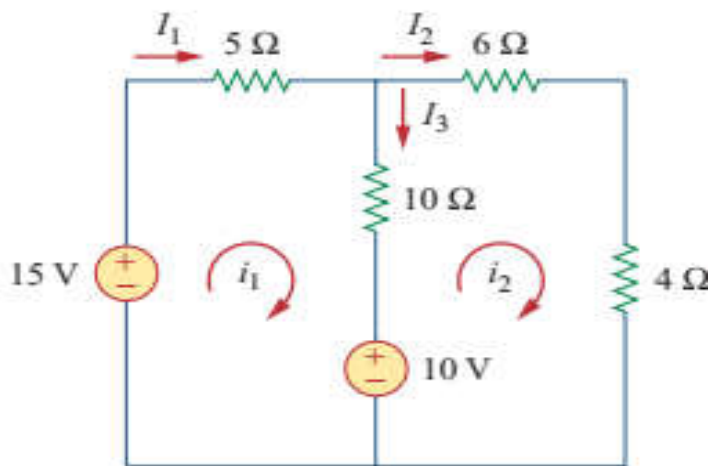Example: For the circuit shown below, find the branch currents  $I_1$ ,  $I_2$ , and  $I_3$  using mesh analysis



**Solution:**

We first obtain the mesh currents using KVL. For mesh 1,

$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

or

$$3i_1 - 2i_2 = 1 \quad \dots(1)$$

For mesh 2,

$$6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$$

or

$$i_1 = 2i_2 - 1 \quad \dots(2)$$

Simplifying the two equations 1, and 2:

$$3i_1 - 2i_2 = 1 \quad \dots (3)$$

$$i_1 - 2i_2 = -1 \quad \dots (4)$$


.....بالطرح

$$2i_1 = 2$$

$$i_1 = 1A$$

$$i_2 = 1A$$

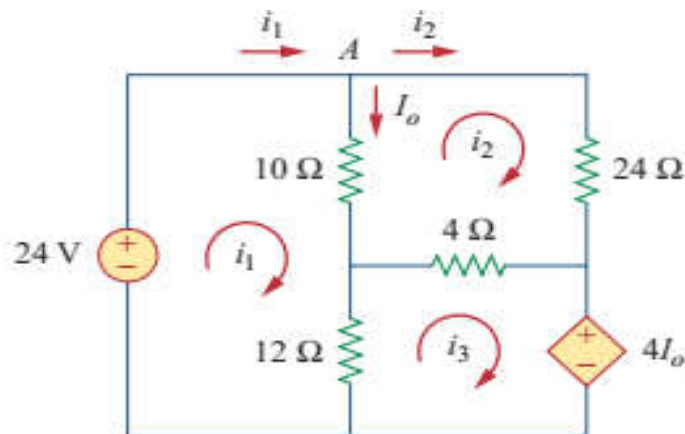Example: use mesh analysis to find the current  $I_o$  for the circuit of figure shown below.



**Solution:**

We apply KVL to the three meshes in turn. For mesh 1,

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$$

or

$$11i_1 - 5i_2 - 6i_3 = 12 \quad \dots(1)$$

For mesh 2,

$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$$

or

$$-5i_1 + 19i_2 - 2i_3 = 0 \quad \dots(2)$$

For mesh 3,

$$4I_o + 12(i_3 - i_1) + 4(i_3 - i_2) = 0 \quad \dots(3)$$

But at node A,  $I_o = i_1 - i_2$ , so that Sub into eq. 3

$$4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

or

$$-i_1 - i_2 + 2i_3 = 0 \quad \dots(4)$$

Solving equations 1, 2, and 4;

$$i_1 = 2.25A$$


$$i_2 = 0.75A$$

$$i_3 = 1.5A$$

$$I_o = i_1 - i_2$$

$$= 2.25 - 0.75 = 1.5A$$

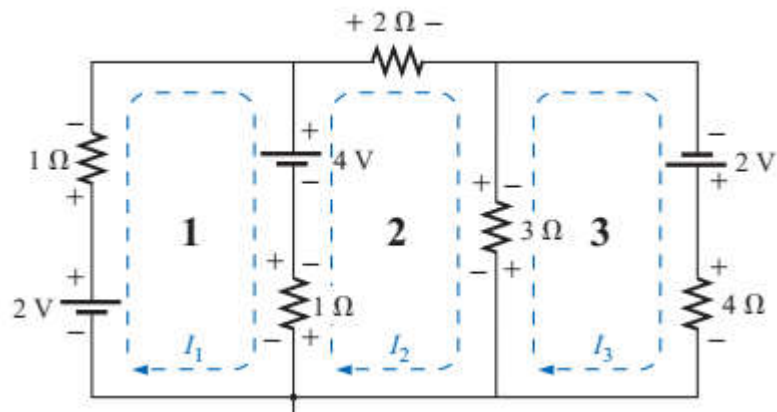Example: Write a mesh equations for the network of figure below:( Format approach)



$I_1$  does not pass through an element mutual with  $I_3$ .

$$\begin{array}{l}
 I_1: \quad (1\ \Omega + 1\ \Omega)I_1 - (1\ \Omega)I_2 + 0 = 2\ \text{V} - 4\ \text{V} \\
 I_2: \quad (1\ \Omega + 2\ \Omega + 3\ \Omega)I_2 - (1\ \Omega)I_1 - (3\ \Omega)I_3 = 4\ \text{V} \\
 I_3: \quad (3\ \Omega + 4\ \Omega)I_3 - (3\ \Omega)I_2 + 0 = 2\ \text{V}
 \end{array}$$


$I_3$  does not pass through an element mutual with  $I_1$ .

Summing terms yields

$$\begin{array}{r}
 2I_1 - I_2 + 0 = -2 \\
 6I_2 - I_1 - 3I_3 = 4 \\
 \underline{7I_3 - 3I_2 + 0 = 2}
 \end{array}$$

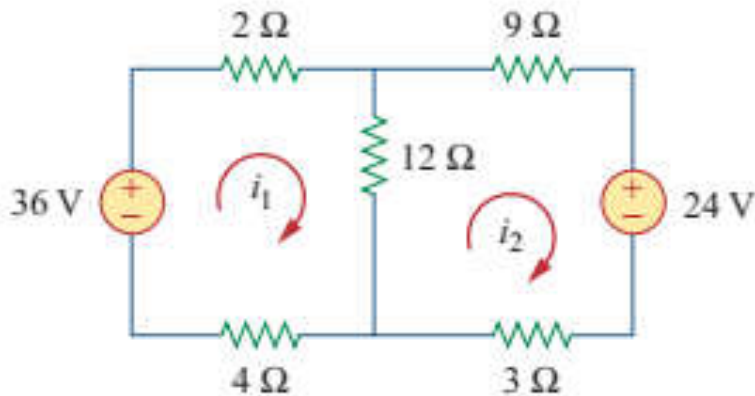
## HW//

- 1- Calculate the mesh currents  $i_1$  and  $i_2$  of the circuit shown below.



**Answer:**  $i_1 = 2 \text{ A}$ ,  $i_2 = 0 \text{ A}$ .

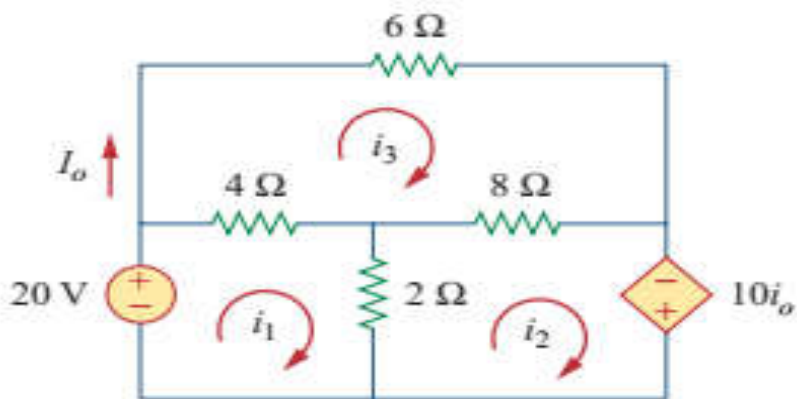- 2- Using mesh analysis, find the current  $I_o$  in the circuit shown below:




**Answer:**  $-5 \text{ A}$ .

- 3- Write a mesh equations for the network of figure of the HW 2 above. ( Format approach)
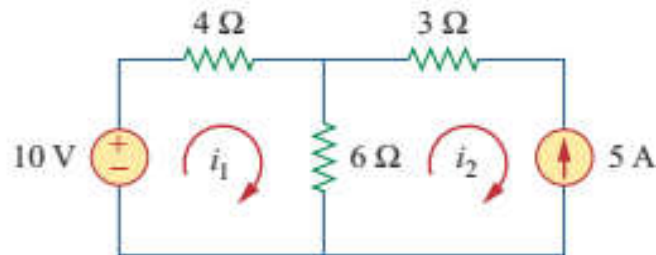
## Mesh Analysis with current source


Case : when a current source exists only in one mesh:

For example see figure below. Set  $i_2 = -5\text{A}$  and write a mesh equation for the other mesh.



$$-10 + 4i_1 + 6(i_1 - i_2) = 0 \quad \Rightarrow \quad i_1 = -2\text{A}$$

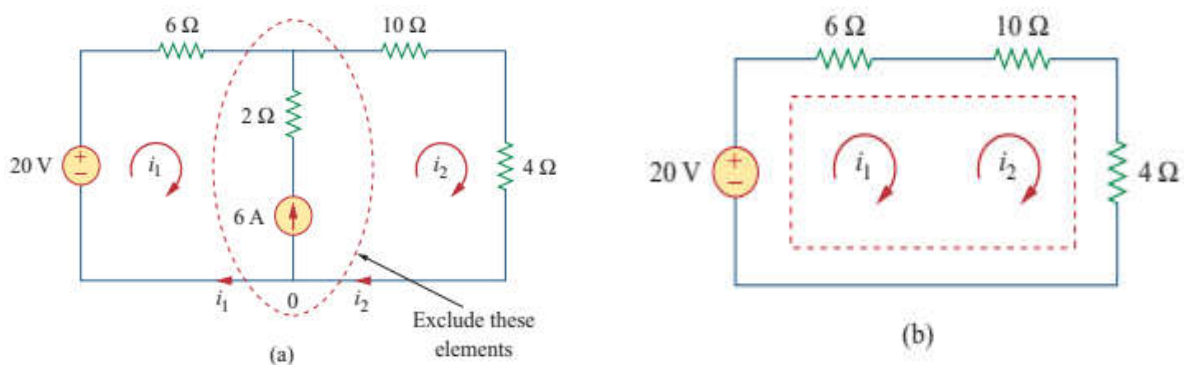Case 2: when a current source exists between two meshes: consider the circuit in figure (a). creating a supermesh by excluding the current source and any elements connected in series with it as shown in figure (b).



A **supermesh** results when two meshes have a (dependent or independent) current source in common.

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0$$


$$6i_1 + 14i_2 = 20$$

$$i_2 - i_1 = 6$$

$$i_2 = i_1 + 6$$


$$i_1 = -3.2 \text{ A}, \quad i_2 = 2.8 \text{ A}$$

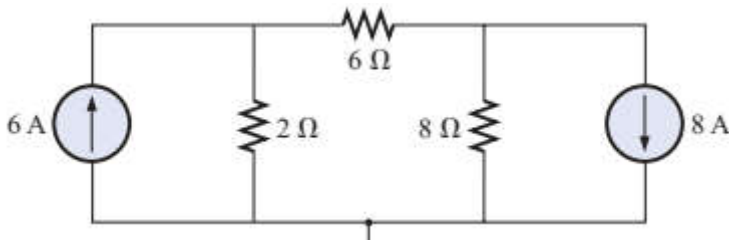Example: using mesh analysis, determine the currents for the network of figure below.




Solution:

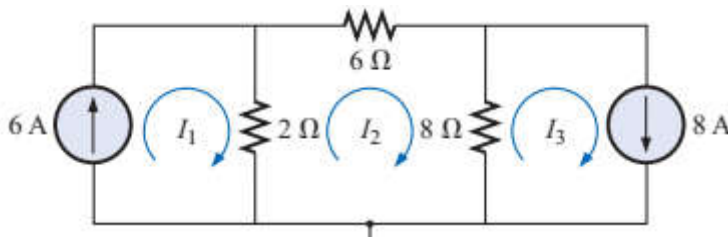The mesh currents are defined in figure (a). The current sources are removed, and the single supermesh path is defined in figure (b)



a

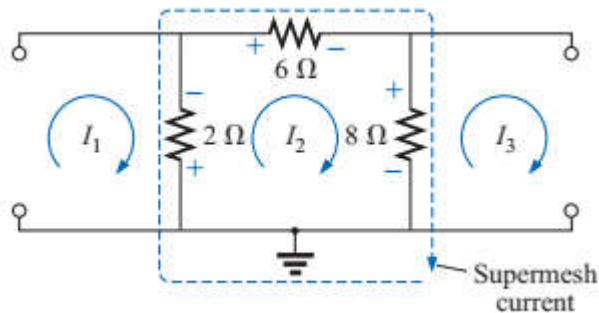

b



$$I_1 = 6A \quad \dots(1)$$

$$I_2 = 8A \quad \dots(2)$$

$$2(I_2 - I_1) + 6I_2 + 8(I_2 - I_3) = 0 \quad \dots(3)$$

results in the following solutions:

$$2I_1 - 16I_2 + 8I_3 = 0$$


$$2(6 A) - 16I_2 + 8(8 A) = 0$$

and 
$$I_2 = \frac{76 A}{16} = 4.75 A$$

Then 
$$I_{2\Omega \downarrow} = I_1 - I_2 = 6 A - 4.75 A = 1.25 A$$

and 
$$I_{8\Omega \uparrow} = I_3 - I_2 = 8 A - 4.75 A = 3.25 A$$

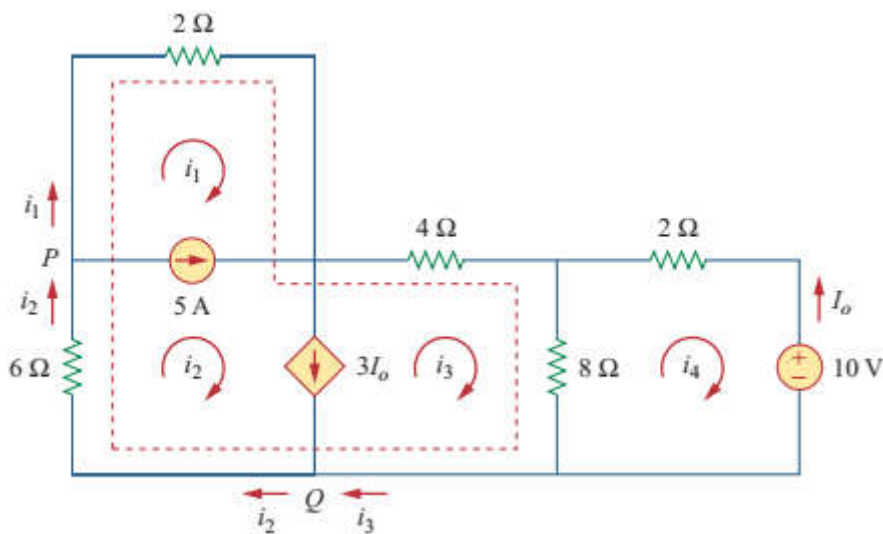Example: for the circuit of figure below, find  $i_1$  to  $i_4$ . using mesh analysis.



$$2i_1 + 4i_3 + 8(i_3 - i_4) + 6i_2 = 0$$

or

$$i_1 + 3i_2 + 6i_3 - 4i_4 = 0$$

For the independent current source, we apply KCL to node  $P$ :

$$i_2 = i_1 + 5$$

For the dependent current source, we apply KCL to node  $Q$ :

$$i_2 = i_3 + 3I_o$$

But  $I_o = -i_4$ , hence,

$$i_2 = i_3 - 3i_4$$

Applying KVL in mesh 4,

$$2i_4 + 8(i_4 - i_3) + 10 = 0$$

or


$$5i_4 - 4i_3 = -5$$

$$i_1 = -7.5 \text{ A}, \quad i_2 = -2.5 \text{ A}, \quad i_3 = 3.93 \text{ A}, \quad i_4 = 2.143 \text{ A}$$

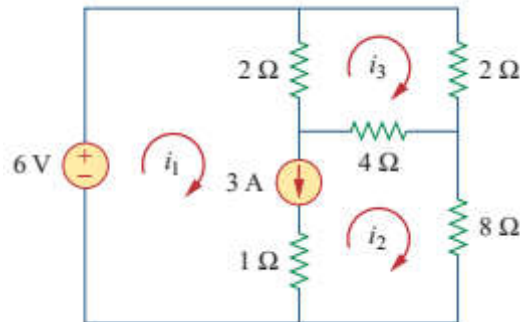
## HW//

- 1- Use mesh analysis to determine  $i_1$ ,  $i_2$ , and  $i_3$  in figure below.

**Answer:**  $i_1 = 3.474 \text{ A}$ ,  $i_2 = 0.4737 \text{ A}$ ,  $i_3 = 1.1052 \text{ A}$ .



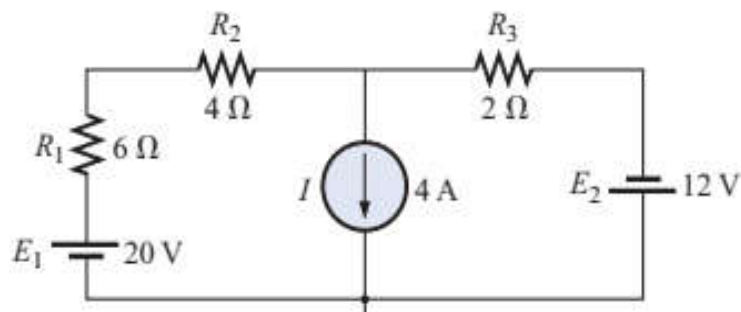- 2- Use mesh analysis, determine the current of figure below.



[Ans.  $I_1=3.33\text{A}$ ,  $I_2=-0.67\text{A}$ ]

47. For the circuit of Fig. 4.76, determine the value of resistor  $X$  if  $i_2 = 2.273$  A.

