

Chapter Three



Network Theorem

- Superposition.
- Thevenen's Theorem
- Norton's Theorem
- Maximum Power Transfer

Superposition Theorem

The **superposition** principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.

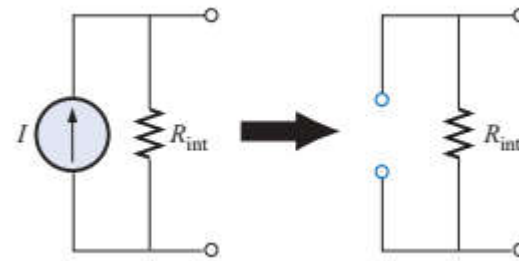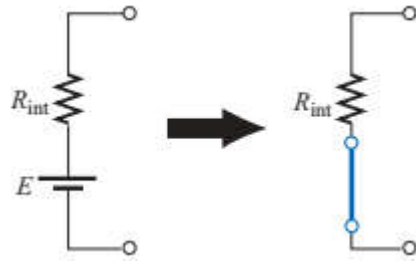1. We consider one independent source at a time while all other independent sources are *turned off*. This implies that we replace every voltage source by 0 V (or a short circuit), and every current source by 0 A (or an open circuit). This way we obtain a simpler and more manageable circuit.
2. Dependent sources are left intact because they are controlled by circuit variables.




Steps to apply superposition principle:

- 1- Turn off all independent sources except one source. Find the output(voltage or current) due to that active source using the - techniques covered in chapter 1 and 2.
- 2-Repeat step 1 for each of the other independent sources.
- 3- Find the total contribution by adding algebraically all the contributions due to the independent sources.



$\text{Number of networks to be analyzed} = \text{Number of independent sources}$

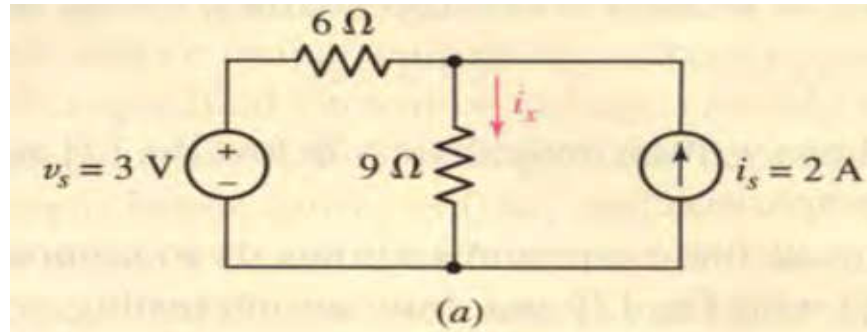Example: For the circuit of figure below, use superposition to write an expression for the unknown branch current i_x .



Solution: The portion of i_x due to voltage source has been designate i'_x (fig.(b)) to avoid the confusion. And due to current source is i''_x fig.(c).

$$i_x = i_x|_{3\text{ V}} + i_x|_{2\text{ A}} = i'_x + i''_x$$

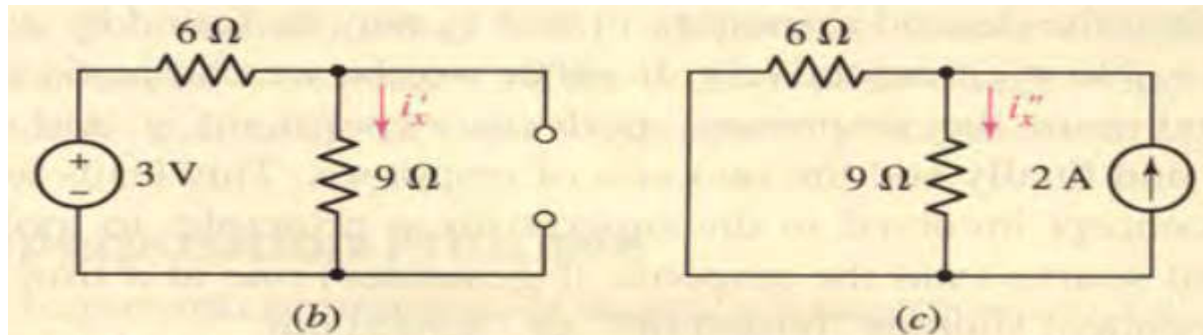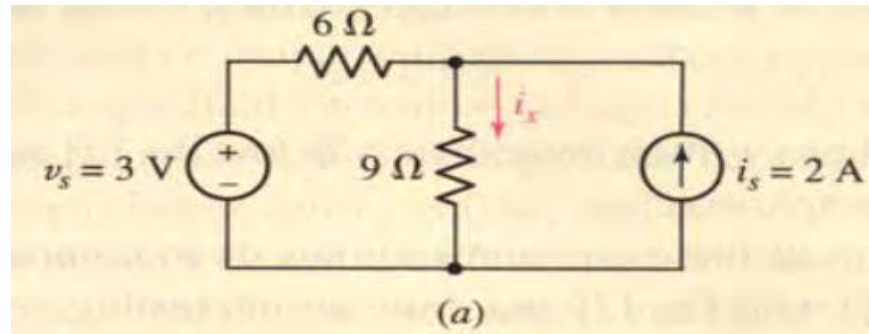


$$i'_x = \frac{3}{6 + 9} = 0.2A$$

$$i''_x = 2 * \frac{6}{6 + 9} = 0.8A$$

$$i_x = 0.2 + 0.8 = 1A$$

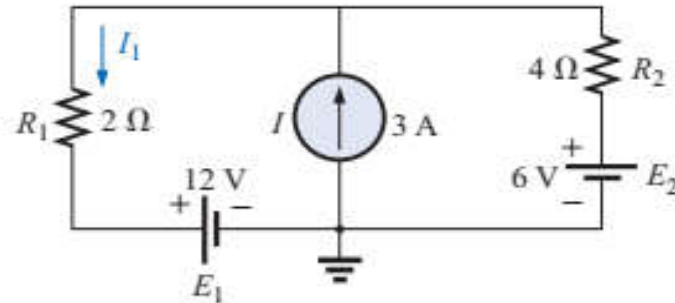Example: Find the current through the $2\ \Omega$ resistor of the network of figure below, using superposition theorem.



The presence of three sources will result in three different networks to be analyzed.


$$I_1 = I_1' + I_1'' + I_1'''$$

I_1' = due to $12\ \text{V}$ voltage source.


I_1'' = due to $6\ \text{V}$ voltage source.

I_1''' = due to $3\ \text{A}$ current source.

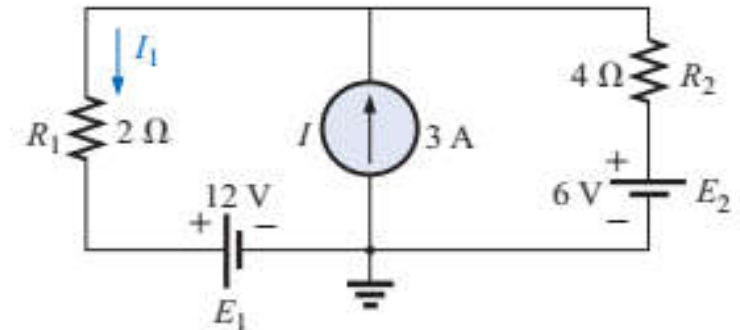1- For the effect of the 12v voltage source.



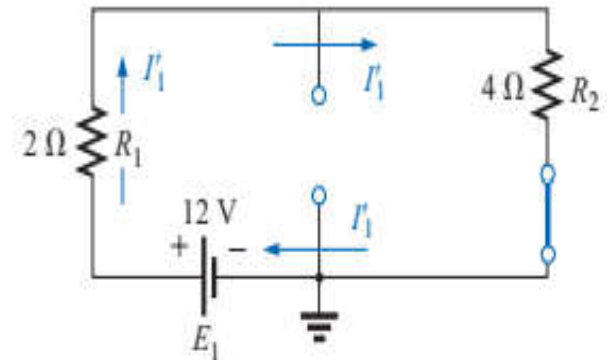
$$I'_1 = \frac{E_1}{R_1 + R_2} = \frac{12 \text{ V}}{2 \Omega + 4 \Omega} = \frac{12 \text{ V}}{6 \Omega} = 2 \text{ A}$$




2- For the effect of the 6v voltage source.
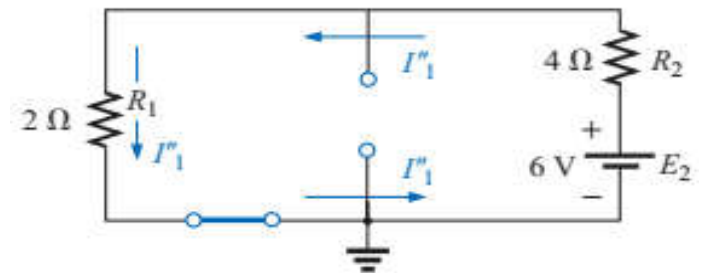
$$I''_1 = \frac{E_2}{R_1 + R_2} = \frac{6 \text{ V}}{2 \Omega + 4 \Omega} = \frac{6 \text{ V}}{6 \Omega} = 1 \text{ A}$$




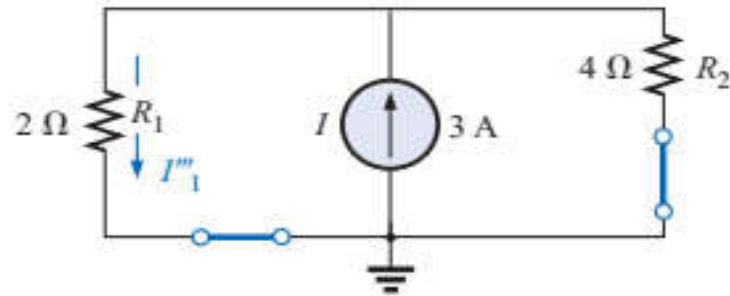
3- For the effect of the 3A current source.



$$I'''_1 = \frac{R_2 I}{R_1 + R_2} = \frac{(4 \Omega)(3 \text{ A})}{2 \Omega + 4 \Omega} = \frac{12 \text{ A}}{6} = 2 \text{ A}$$

The total current through the 2Ω resistor appears in figure below:

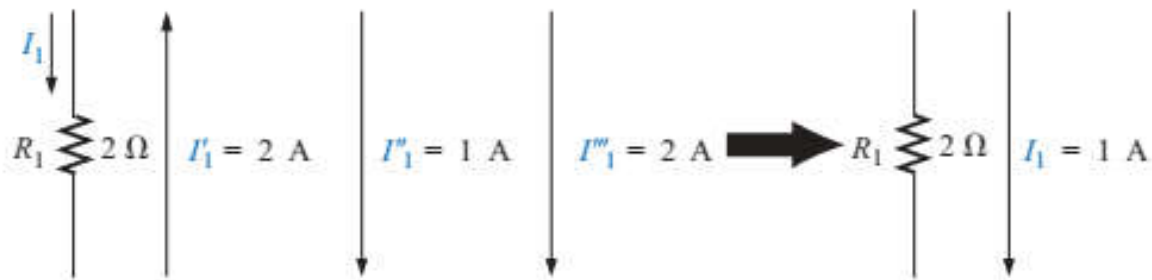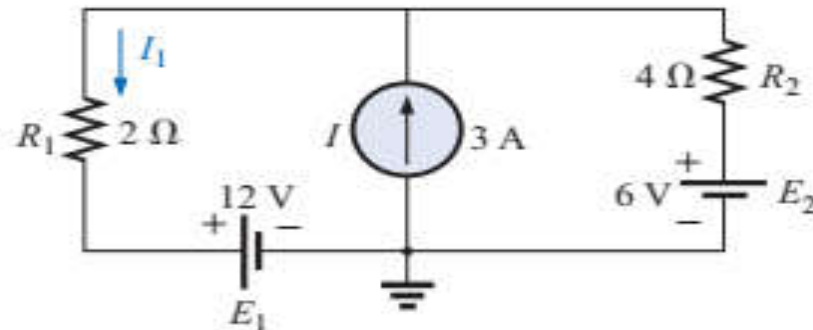The total current through the 2Ω resistor appears in figure below:



Same direction
as I_1 in Fig. 9.19

Opposite direction
to I_1 in Fig. 9.19

$$\begin{aligned}
 I_1 &= \overbrace{I''_1 + I'''_1} - I'_1 \\
 &= 1\text{A} + 2\text{A} - 2\text{A} = 1\text{A}
 \end{aligned}$$

Example: Find the value of I_o in the circuit shown below, using superposition.



$$i_o = i'_o + i''_o$$

Where

i'_o is due to the 4A current source

i''_o is due to the 20V voltage source.

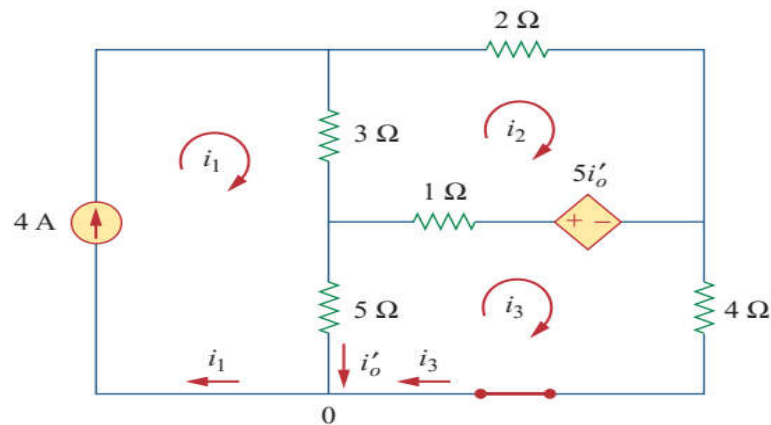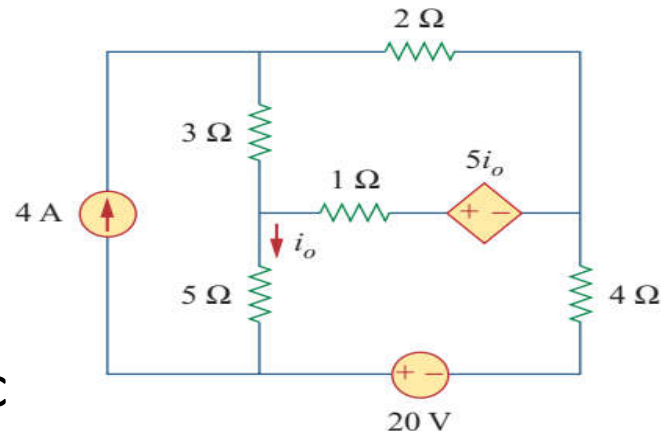To obtain i'_o , the 20V voltage source is turned off.



Now, apply mesh analysis in order to obtain i_o' .

For mesh 1:-

$$i_1 = 4 \text{ A} \quad \dots(1)$$

For mesh 2:-


$$-3i_1 + 6i_2 - 1i_3 - 5i_o' = 0 \quad \dots(2)$$

For mesh 3:-

$$-5i_1 - 1i_2 + 10i_3 + 5i_o' = 0 \quad \dots(3)$$

At node o,
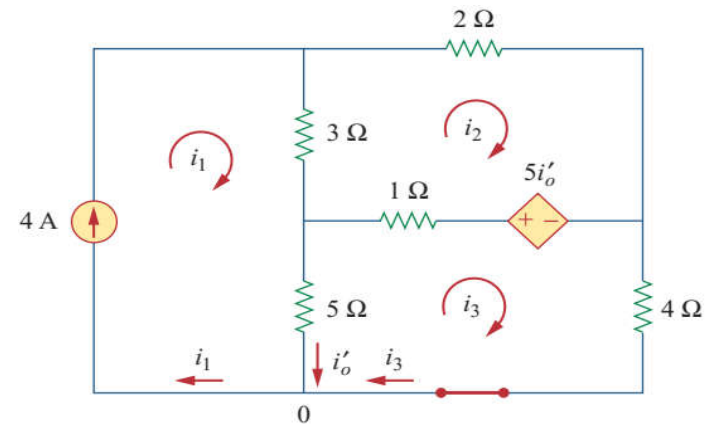
$$i_3 = i_1 - i_o' = 4 - i_o' \quad \dots(4)$$



Sub. 1, and 4 into 2

$$3i_2 - 2i'_o = 8$$

$$i_2 + 5i'_o = 20$$

which can be solved to get


$$i'_o = \frac{52}{17} \text{ A}$$

To obtain i_o'' , the 4A current source is turned off.

$$6i_4 - i_5 - 5i_o'' = 0$$

$$-i_4 + 10i_5 - 20 + 5i_o'' = 0$$

$$\text{But } i_5 = -i_o''.$$

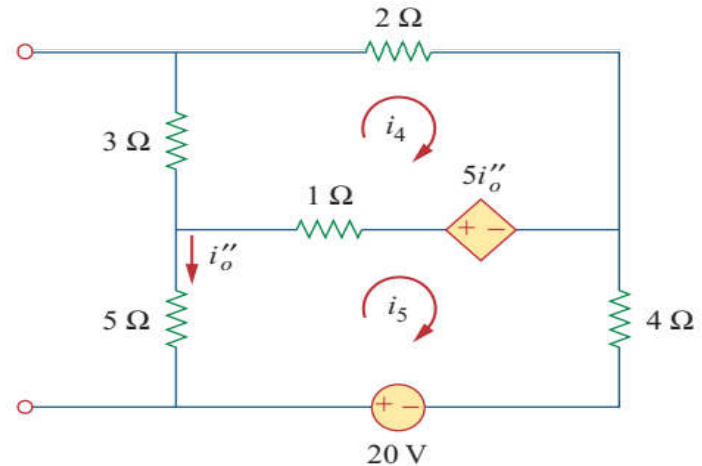

$$6i_4 - 4i''_o = 0$$


$$i_4 + 5i''_o = -20$$

which we solve to get

$$i''_o = -\frac{60}{17} \text{ A}$$


$$i_o = i'_o + i''_o$$
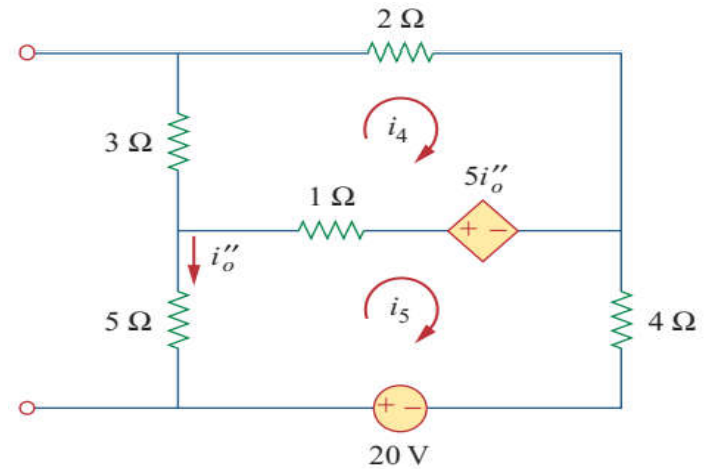
$$i_o = -\frac{8}{17} = -0.4706 \text{ A}$$




HW

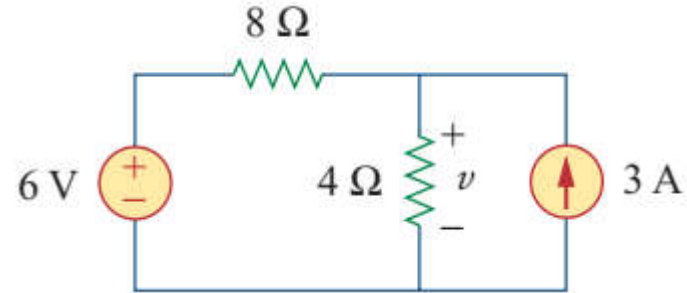
1- Use superposition theorem to find the voltage v in the circuit shown below.



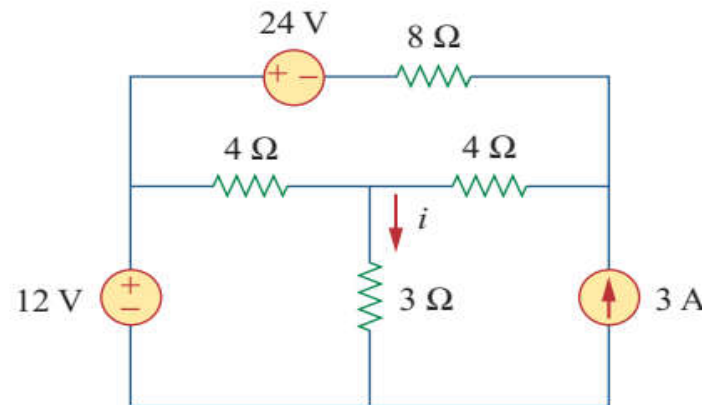2- For the circuit shown below, find the value of i , using superposition theorem.



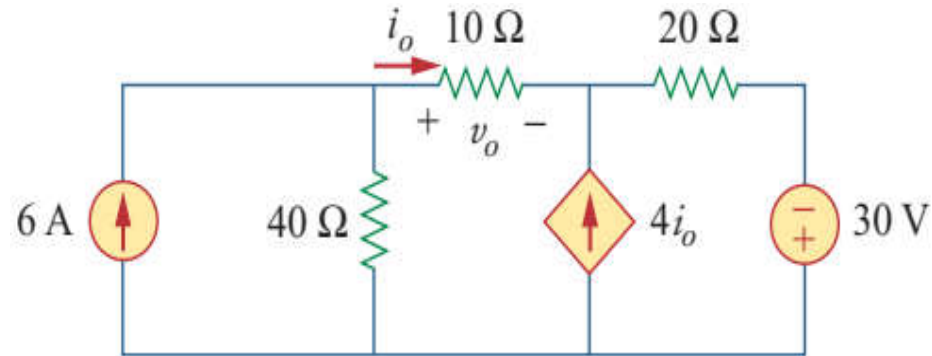3- Use superposition theorem, find the value of v_o and i_o in the circuit shown below.



4- Referring to the circuit of Fig. 5.5a, determine the maximum *positive* current to which the source I_x can be set before any resistor exceeds its power rating and overheats.

