
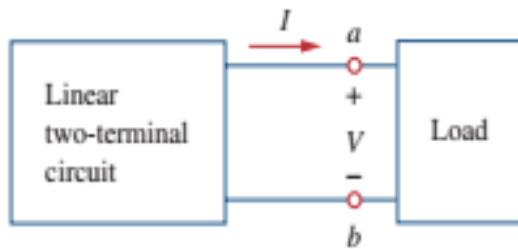


Thevenin's Theorem

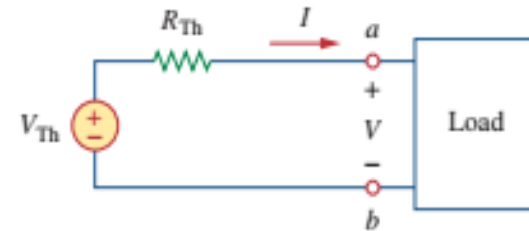


(a)



(b)


Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{Th} in series with a resistor R_{Th} , where V_{Th} is the open-circuit voltage at the terminals and R_{Th} is the input or equivalent resistance at the terminals when the independent sources are turned off.

$$V_{Th} = v_{oc}$$

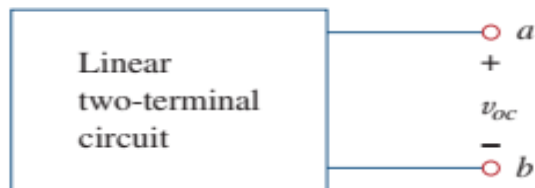

$$V_{Th} = v_{oc}$$


(a)

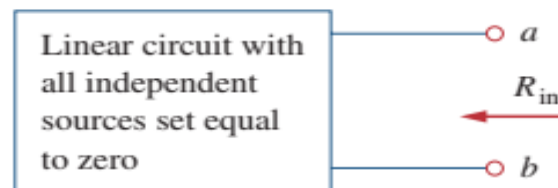


$$R_{Th} = R_{in}$$

(b)

- For example

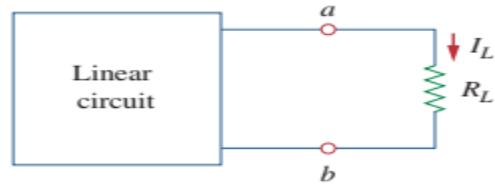

(a)

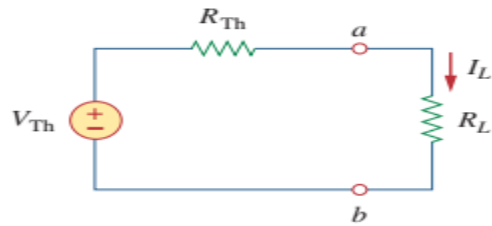


(b)

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$

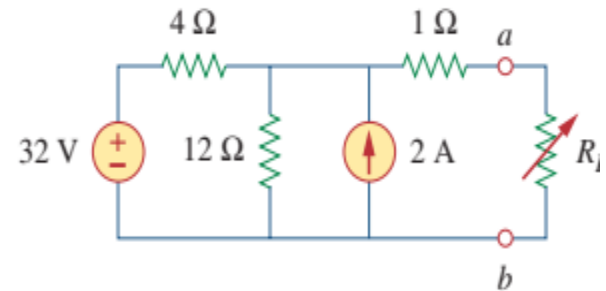Example(1):


Find the equivalent circuit of the circuit shown in the figure below, to the left of the terminals (a-b), then find the current through $R_L = 6\Omega$.





Solution:

We find R_{Th} by turning off the 32-V voltage source (replacing it with a short circuit) and the 2-A current source (replacing it with an open circuit). The circuit becomes what is shown in Fig.
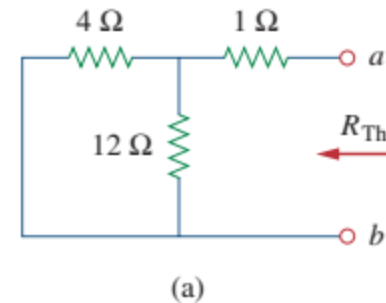
$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{16} + 1 = 4 \Omega$$



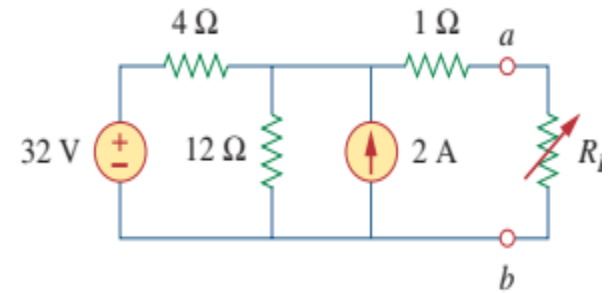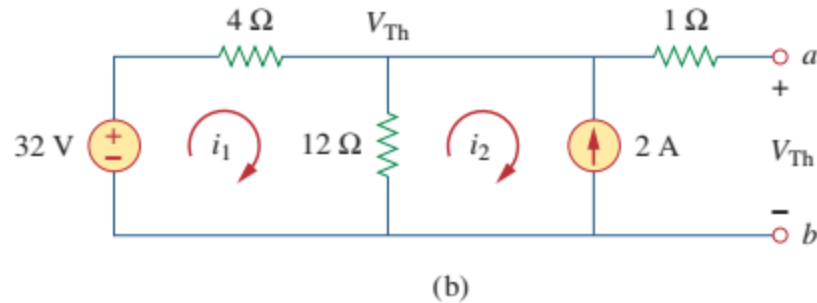- To find V_{th} , consider the circuit in figure below, Applying mesh analysis to the two loops, we obtain:



$$-32 + 4i_1 + 12(i_1 - i_2) = 0, \quad i_2 = -2 \text{ A}$$

Solving for i_1 , we get $i_1 = 0.5 \text{ A}$. Thus,


$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30 \text{ V}$$

- The thevenins equivalent circuit is shown below, and the current (I_L) through the R_L is :



$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L}$$

When $R_L = 6$,

$$I_L = \frac{30}{10} = 3 \text{ A}$$

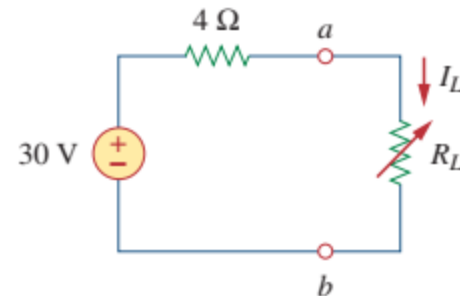


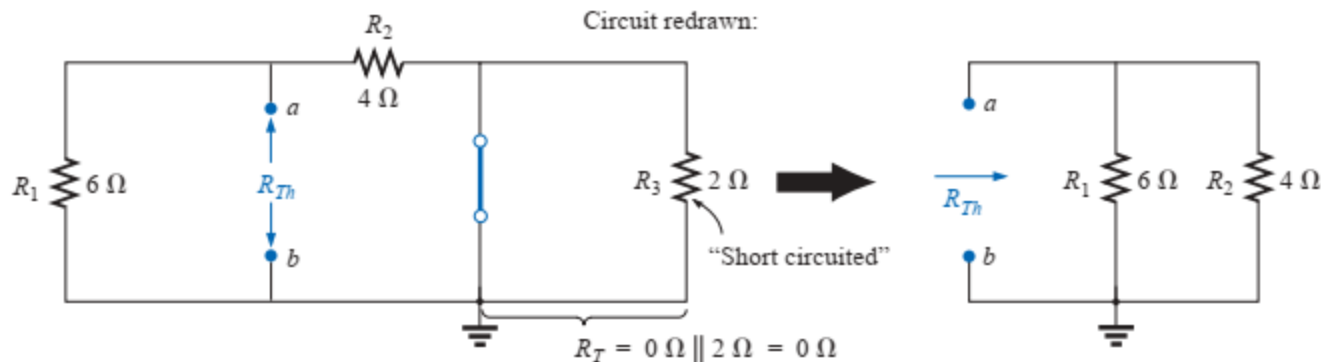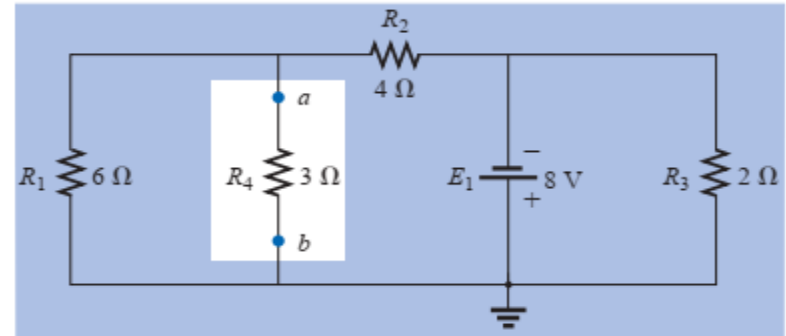Example(2): Find the Thevenin's equivalent circuit for the network in the shaded area of the network of figure below.




$$R_{Th} = R_1 \parallel R_2 = \frac{(6\ \Omega)(4\ \Omega)}{6\ \Omega + 4\ \Omega} = \frac{24\ \Omega}{10} = 2.4\ \Omega$$

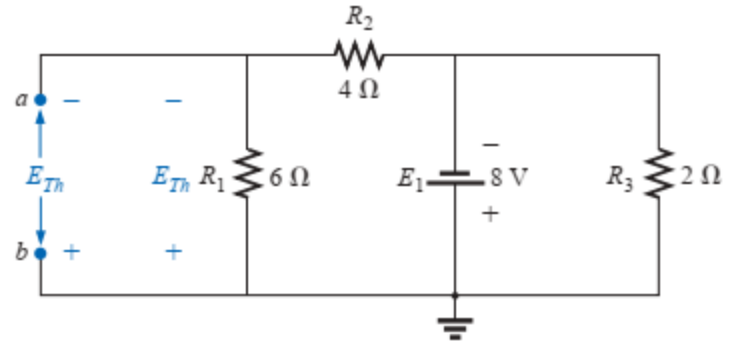
$$E_{Th} = \frac{R_1 E_1}{R_1 + R_2} = \frac{(6 \Omega)(8 \text{ V})}{6 \Omega + 4 \Omega} = \frac{48 \text{ V}}{10} = 4.8 \text{ V}$$



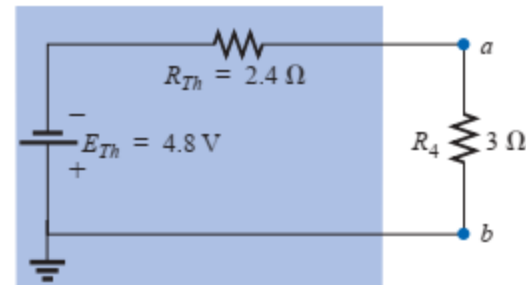
$$I = \frac{E_{TH}}{(R_{TH} + R_4)} = \frac{4.8}{2.4 + 3} = 0.89 \text{ A}$$



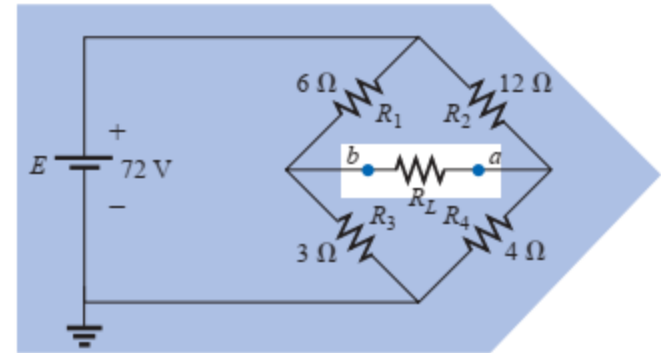Example (3): For the circuit shown in the figure below, find the Thevenin's equivalent circuit



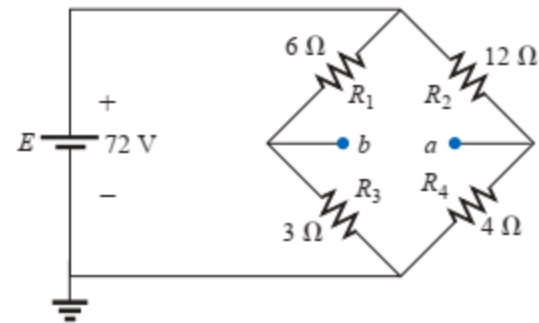
$$\begin{aligned}
 R_{Th} = R_{a-b} &= R_1 \parallel R_3 + R_2 \parallel R_4 \\
 &= 6 \Omega \parallel 3 \Omega + 4 \Omega \parallel 12 \Omega \\
 &= 2 \Omega + 3 \Omega = 5 \Omega
 \end{aligned}$$



$$V_1 = \frac{R_1 E}{R_1 + R_3} = \frac{(6 \Omega)(72 \text{ V})}{6 \Omega + 3 \Omega} = \frac{432 \text{ V}}{9} = 48 \text{ V}$$
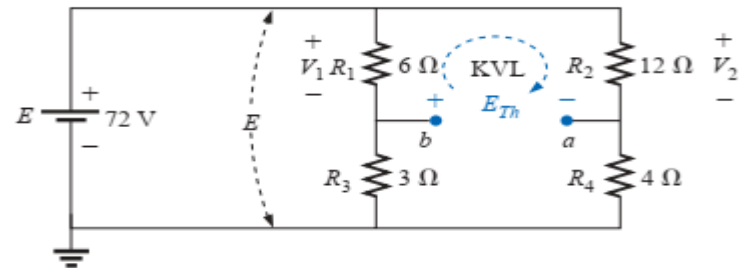
$$V_2 = \frac{R_2 E}{R_2 + R_4} = \frac{(12 \Omega)(72 \text{ V})}{12 \Omega + 4 \Omega} = \frac{864 \text{ V}}{16} = 54 \text{ V}$$




Assuming the polarity shown for E_{Th} and applying Kirchhoff's voltage law to the top loop in the clockwise direction will result in

$$\sum_C V = +E_{Th} + V_1 - V_2 = 0$$

and $E_{Th} = V_2 - V_1 = 54 \text{ V} - 48 \text{ V} = 6 \text{ V}$



When $R_L = 7 \Omega$,
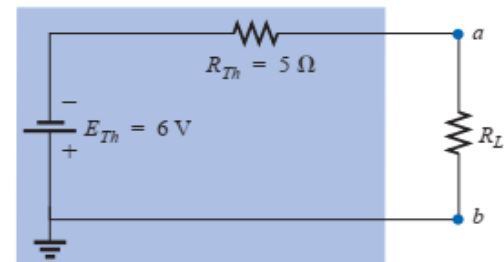
$$I = \frac{E_{TH}}{R_{Tj} + R_L} = \frac{6}{5 + 7} = 0.5 \text{ A}$$




HW

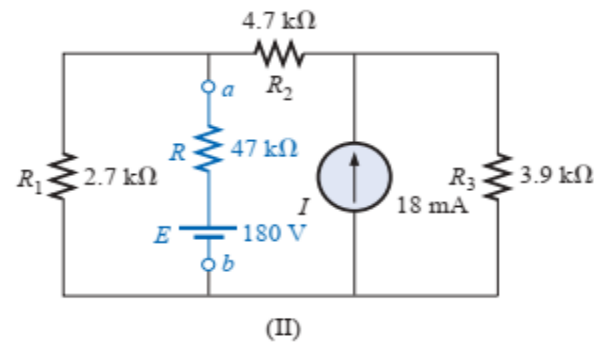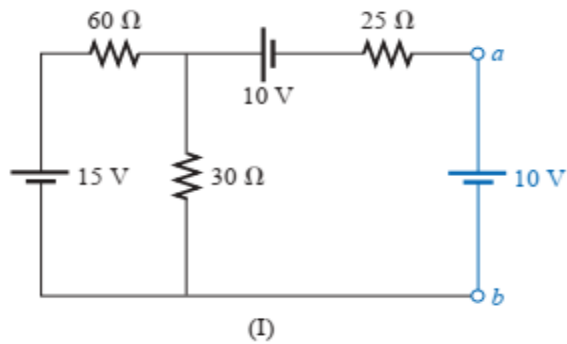
- 1- Find the Thevenin's equivalent circuit for the portions of the networks of figure below at points a and b.



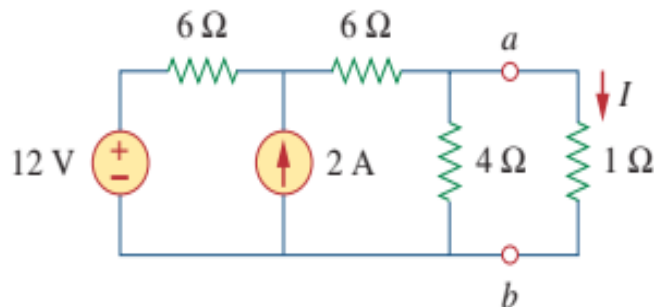- 2- Find the current I using Thevenin's Theorem.



- 3- Find the Thevenin's equivalent

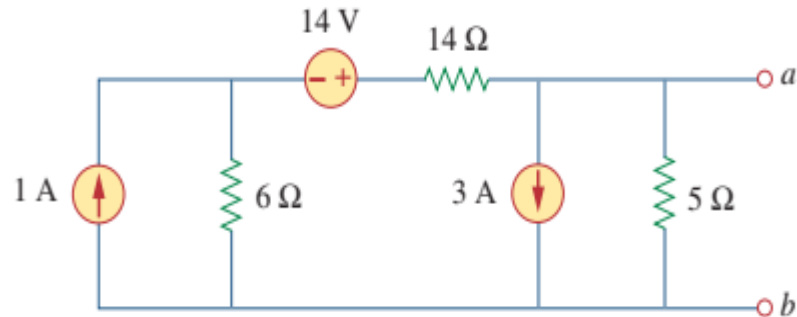

- 4- Find the Thevenin's equivalent circuit for the network within the shaded area of Figure below:.

