

*Basrah University  
College of Engineering  
Electrical Engineering Department*



## **Electric Circuits Analysis**

*Asst. Lect: Hamzah Abdulkareem*

### **Chapter Two**

#### **Part 3**

#### **Transient Circuits**

- ***General Second-Order Circuits***

## Chapter Two

### Transient Circuits

#### 2.12 General Second-Order Circuits

Now that we have mastered series and parallel RLC circuits, we are prepared to apply the ideas to any second-order circuit having one or more independent sources with constant values. Although the series and parallel RLC circuits are the second-order circuits of greatest interest, other second-order circuits are also useful. Given a second-order circuit, we determine its step response  $x(t)$  (which may be voltage or current) by taking the following four steps :-

- 1- We first determine the initial conditions  $x(0)$  and  $\frac{dx(0)}{dt}$  and the final value (steady state value).
- 2- We turn off the independent sources and find the form of the transient response  $x_t(t)$  by applying KCL and KVL. Once a second-order differential equation is obtained, we determine its characteristic roots. Depending on whether the response is overdamped, critically damped, or underdamped, we obtain  $x_t(t)$  with two unknown constants as we did in the previous sections.
- 3- The total response is now found as the sum of the transient response and steady-state response.

$$x(t) = x_t(t) + x_{ss}(t) \quad \dots(2.69)$$

- 4- We finally determine the constants associated with the transient response by imposing the initial conditions  $x(0)$  and  $\frac{dx(0)}{dt}$  determined in step 1.

**Example 2.16:-** Find the complete response  $v(t)$  &  $i(t)$  in circuit in the Fig. 2.39.

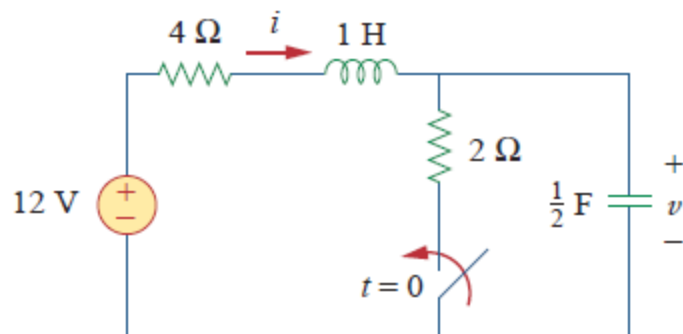


Fig 2.39 For Example 2.16

**Example 2.17:-** Find  $v_o(t)$  for  $t > 0$  in circuit in the Fig. 2.40.

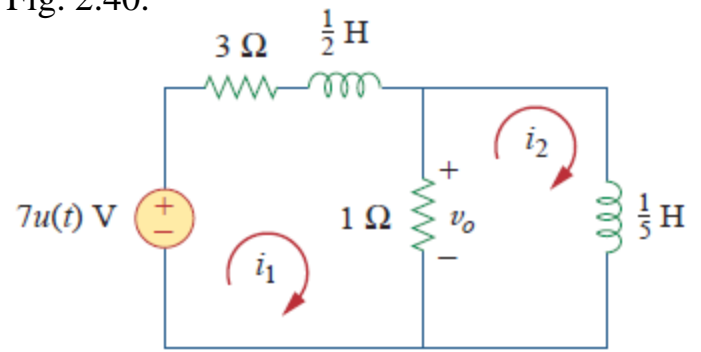


Fig 2.40 For Example 2.17